

DIGITAL SYSTEM DESIGN

Lecture 4


Adders

Waqar Ahmad

Faculty of Computer Science and Engineering

Adding Two One-bit Operands

- One-bit Half Adder:

 


$$\text{Sum} = A \oplus B$$

$$\text{Cout} = A.B$$

A	B	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- One-bit Full Adder:

 


$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = A.B + B.\text{Cin} + A.\text{Cin}$$

$$= A.B + (A \oplus B).\text{Cin}$$

C _{in}	A	B	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
<hr/>				
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Propagation Delay in Full Adders

 

- From A_i or B_i to C_{i+1} : 4 gate-delays (XOR \rightarrow AND \rightarrow OR)
- From A_i or B_i to S_i : 4 gate-delays (XOR \rightarrow XOR)
- From C_i to C_{i+1} : 2 gate-delays (AND \rightarrow OR)
- From C_i to S_i : 2 gate-delays (XOR)

Ripple Carry Adder

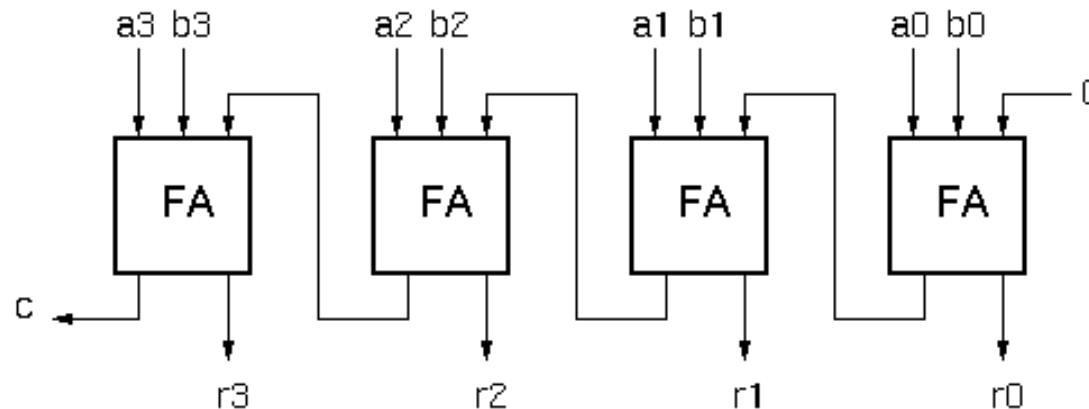
- Constructed by cascading full adders (FA) blocks in series
- A 4-bit carry ripple adder is shown below



Delay in Ripple Carry Adders

- Recall: For a full-adder
 - From A_i or B_i to C_{i+1} : 4 gate-delays (XOR \rightarrow AND \rightarrow OR)
 - From A_i or B_i to S_i : 4 gate-delays (XOR \rightarrow XOR)
 - From C_i to C_{i+1} : 2 gate-delays (AND \rightarrow OR)
 - From C_i to S_i : 2 gate-delays (XOR)
- In ripple carry adder, the carry-out of one FA is the carry-in of next FA, the worst-case propagation delay is then:
 - 4 gate-delays from generating the first carry signal ($A_0/B_0 \rightarrow C_1$).
 - 2 gate-delays per intermediate stage ($C_i \rightarrow C_{i+1}$).
 - 2 gate-delays at the last stage to produce both the sum and carry-out outputs ($C_{n-1} \rightarrow C_n$ and S_{n-1}).


4-bit Ripple Carry Addition: Example

 

T=0	0	0	0	0	0	0	0	0	S=0000
T=1	0	0	0	1	0	1	1	0	S=0110
T=2	0	0	0	1	1	0	1	0	S=0100
T=3	0	0	1	0	1	0	1	0	S=0000
T=4	0	1	1	0	1	0	1	0	S=1000

Critical Path Through a Ripple-Carry Adder
 
$$T_{\text{ripple-add}} = T_{\text{FA}}(X \rightarrow s) + (k - 2) \times T_{\text{FA}}(c_{\text{in}} \rightarrow c_{\text{out}}) + T_{\text{FA}}(c_{\text{in}} \rightarrow s)$$



Critical path in a k -bit ripple-carry adder.

Pros and Cons


- Advantages

- Compact layout giving smaller chip area.
- Lower power consumption

- Disadvantages

- Delay increases linearly with increasing bit-length
 - At least 2 gate delays for every additional bit


Carry Skip (Bypass) Adder

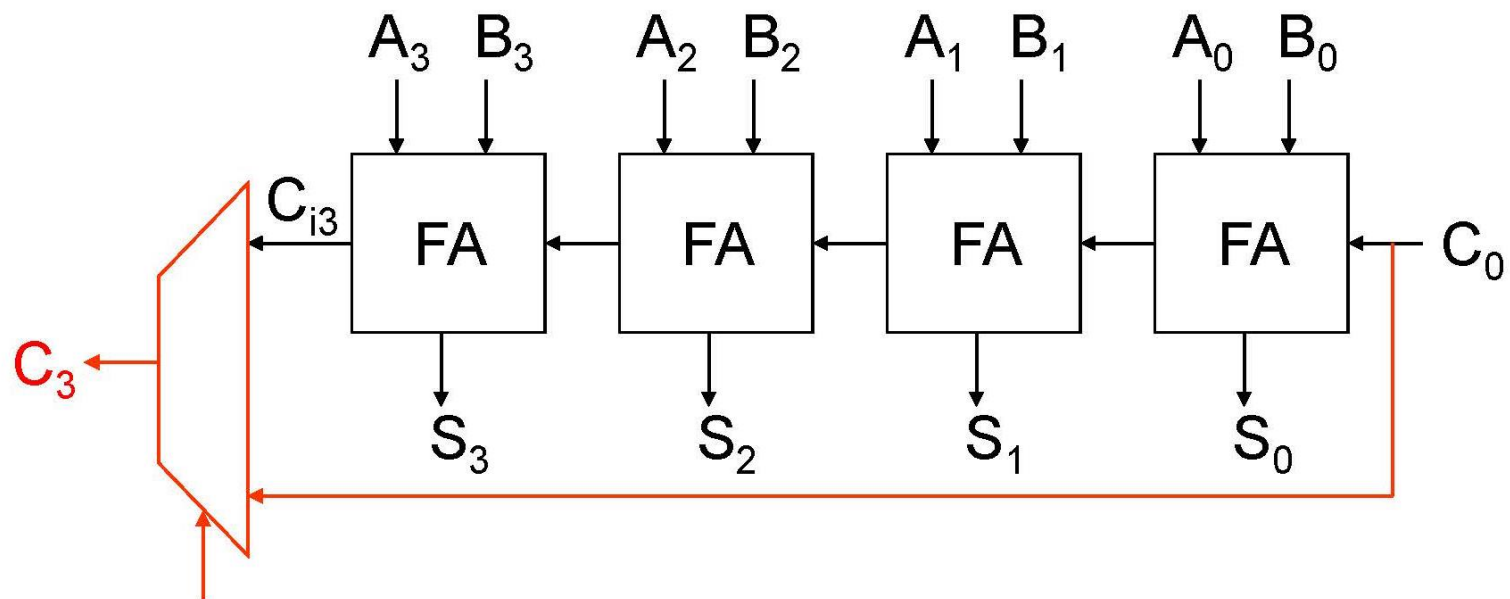


$BP = P_0 P_1 P_2 P_3$ (Block Propagate)

if $(P_0 P_1 P_2 P_3) C_3 = C_0$
 else $C_3 = C_{i3}$

 16-bit Carry Skip Adder using 4-bit blocks




Carry Skip Adder – Delay

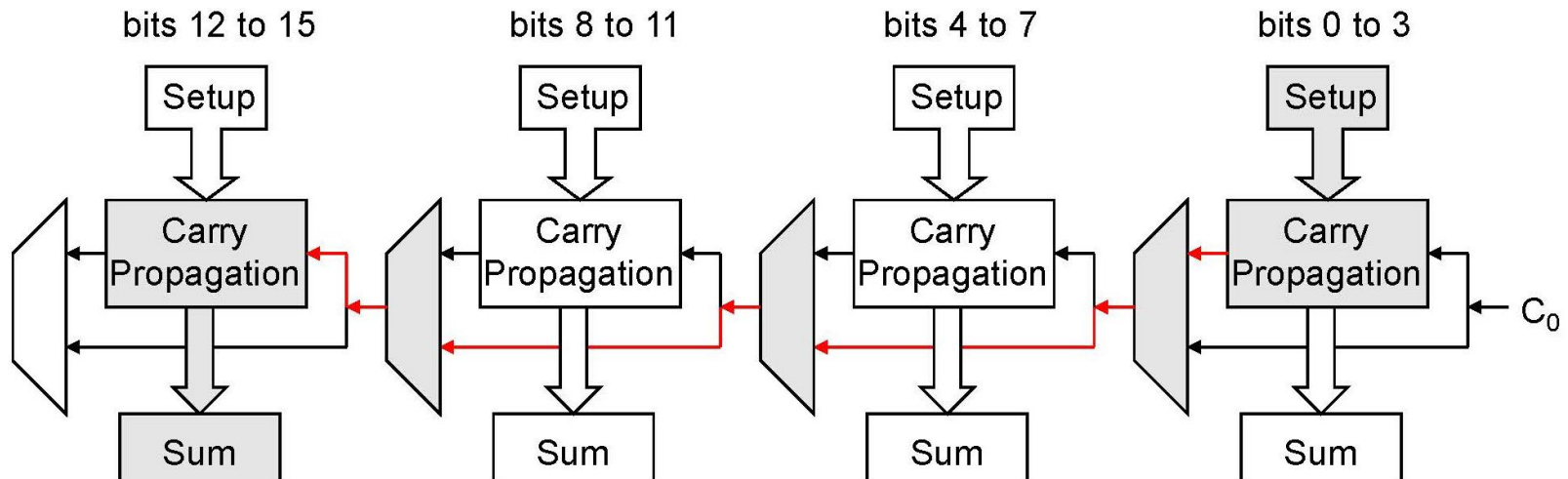

worst-case delay = carry from bit 0 to bit 15 = carry generated in bit 0, **ripples** through bits 1, 2, and 3, **skips** the middle two groups (M is the group size in bits), **ripples** in the last group from bit 12 to bit 15

$$t_{\text{add}} = t_{\text{setup}} + M t_{\text{carry}} + ((N/M) - 1) t_{\text{skip}} + (M-1) t_{\text{carry}} + t_{\text{sum}}$$

 Delay – Carry Skip Adder vs Ripple Carry Adder




Carry Select Adder

- Do we have to wait for the previous-carry to show up to compute next sum and carry?
 - We do have to know the carry to get the right answer.
 - But, **it can only take on two values**
- **Idea:** Compute both possible values and select correct result when we know the actual input
- Principle:
 - The adder is partitioned into M groups
 - Two values of sum with cin (1 and 0) are pre computed for each adder group
 - Actual sum is selected using a 2-to-1 MUX by the carry of the previous group
 - **Compute possible results in parallel**
 - **Select when actual carry-in available**
 - Requires internal carry for blocks, e.g. ripple effected by block sizing


Ways of Implementation

- Levels
 - 1 – Level
 - N – Level
- Grouping
 - Uniform Group
 - Non-Uniform Group

One-level k-bit Carry-Select Adder

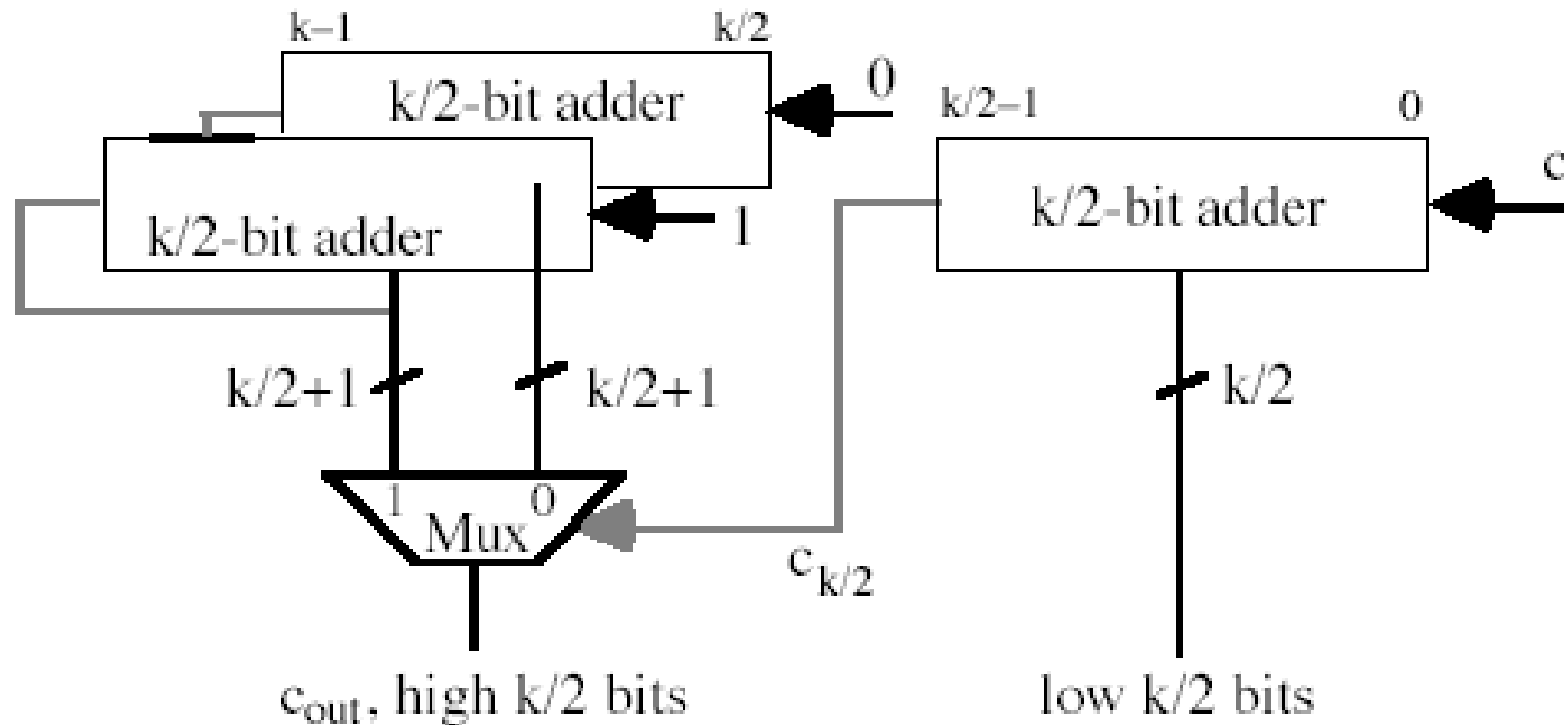


1-Level 8-bit Uniform Carry Select Adder

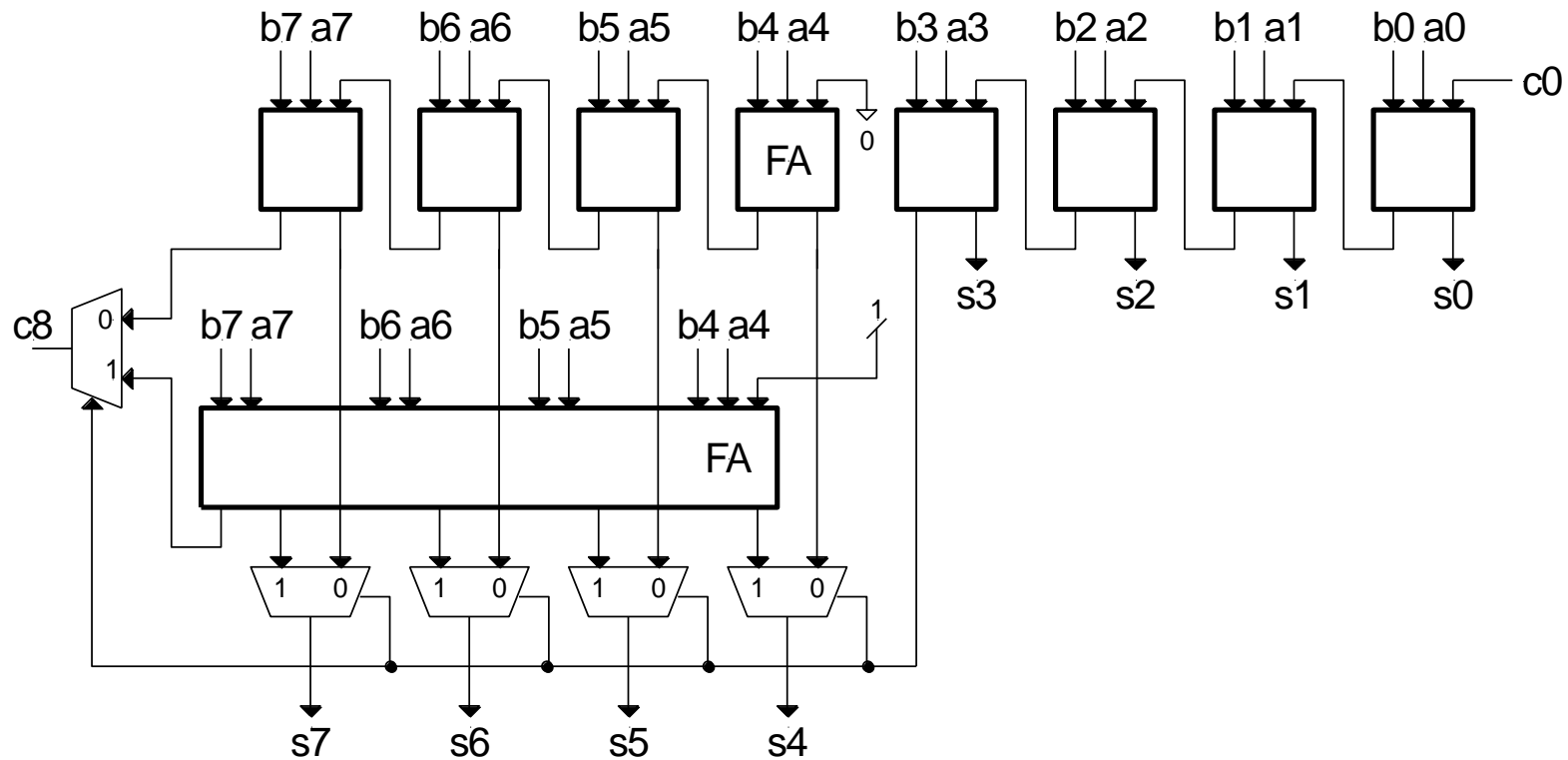


$$T = T_{4\text{bit_ripple_adder}} + T_{\text{MUX}}$$

1-Level 16-bit Uniform Carry Select Adder

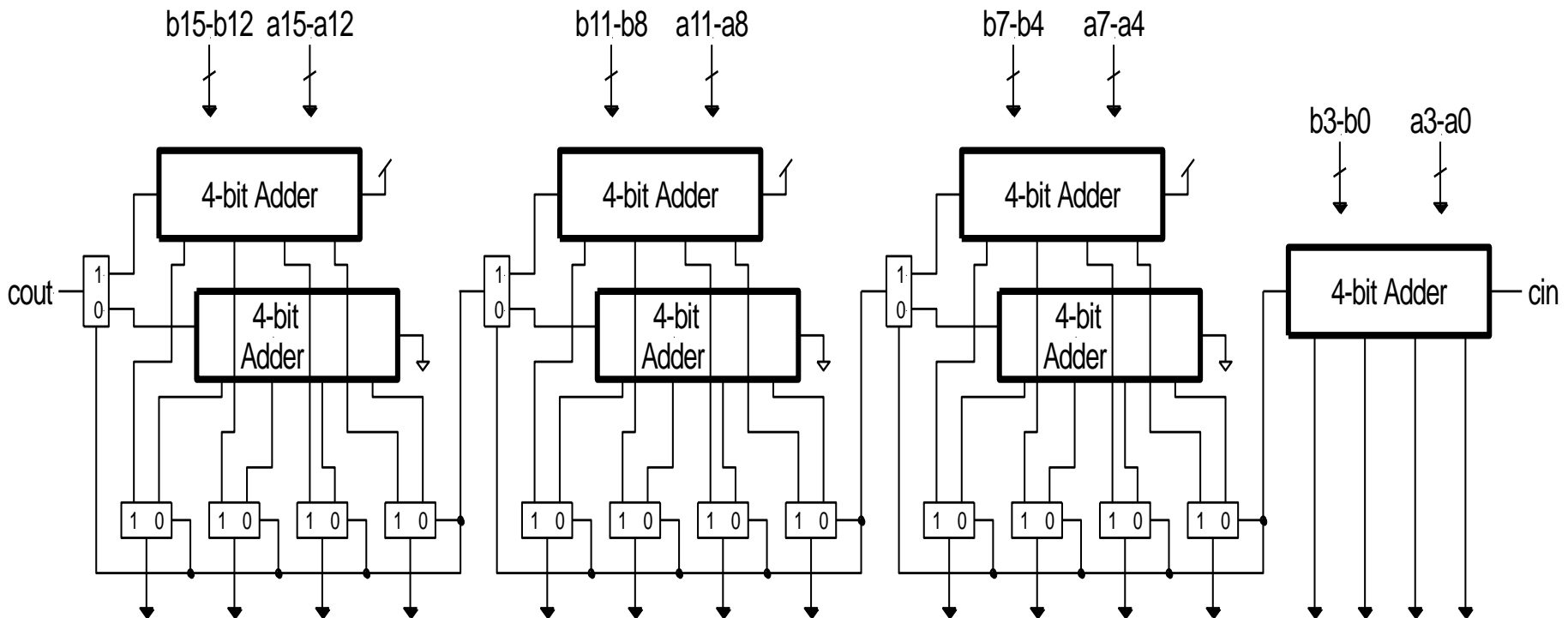- Extending Carry-select to multiple blocks
- What is the optimal # of blocks and # of bits/block?
 - If # blocks too large delay dominated by total mux delay
 - If # blocks too small delay dominated by adder delay




Uniform Carry Select Adder: Timing

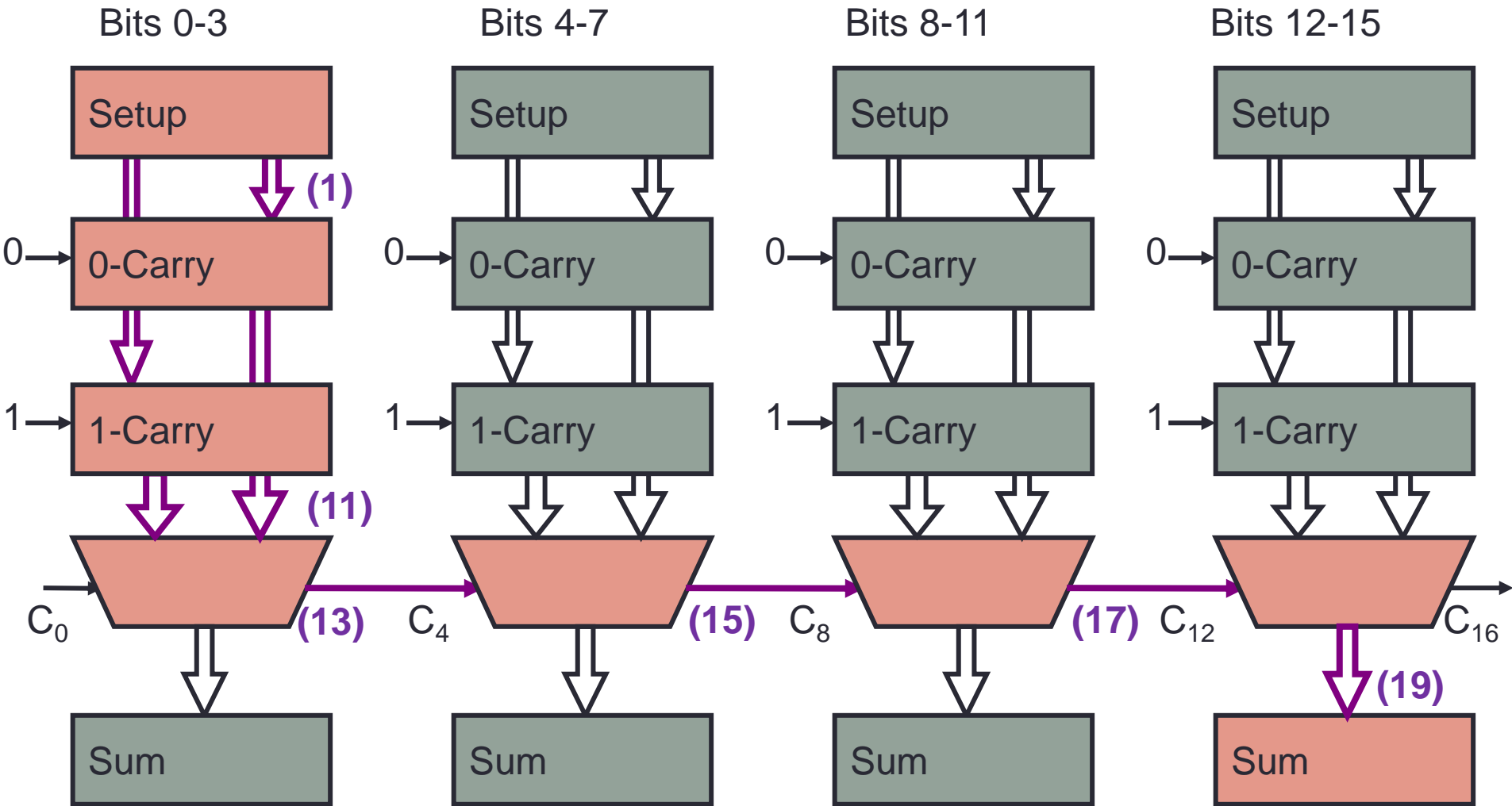

Non-Uniform Carry Select Adder

- Later stages have to wait for the multiplexers in the earlier stages
- Why not give them bigger chunks of data to compute?
 - Balances the delay paths
 - Sub-linear delay (we will see why)

 
Non-Uniform Carry Select Adder: The Structure



$$\text{Delay} = 1 + 6 + 2 + 2 + 2 + 2 + 2 = 17 (16 \text{ bits})$$

The numbers in the block indicate number of bits processed in that block.


Non-Uniform Carry Select Adder: 20-bits

 


$$\text{Delay} = 1 + 6 + 2 + 2 + 2 + 2 + 2 = 17 \text{ (20 bits)}$$

Note how the numbers of bits pre-computed by each stage progressively increase.

 Delay – Carry Select Adder vs Ripple Carry Adder




Two-level k-bit Carry Select Adder

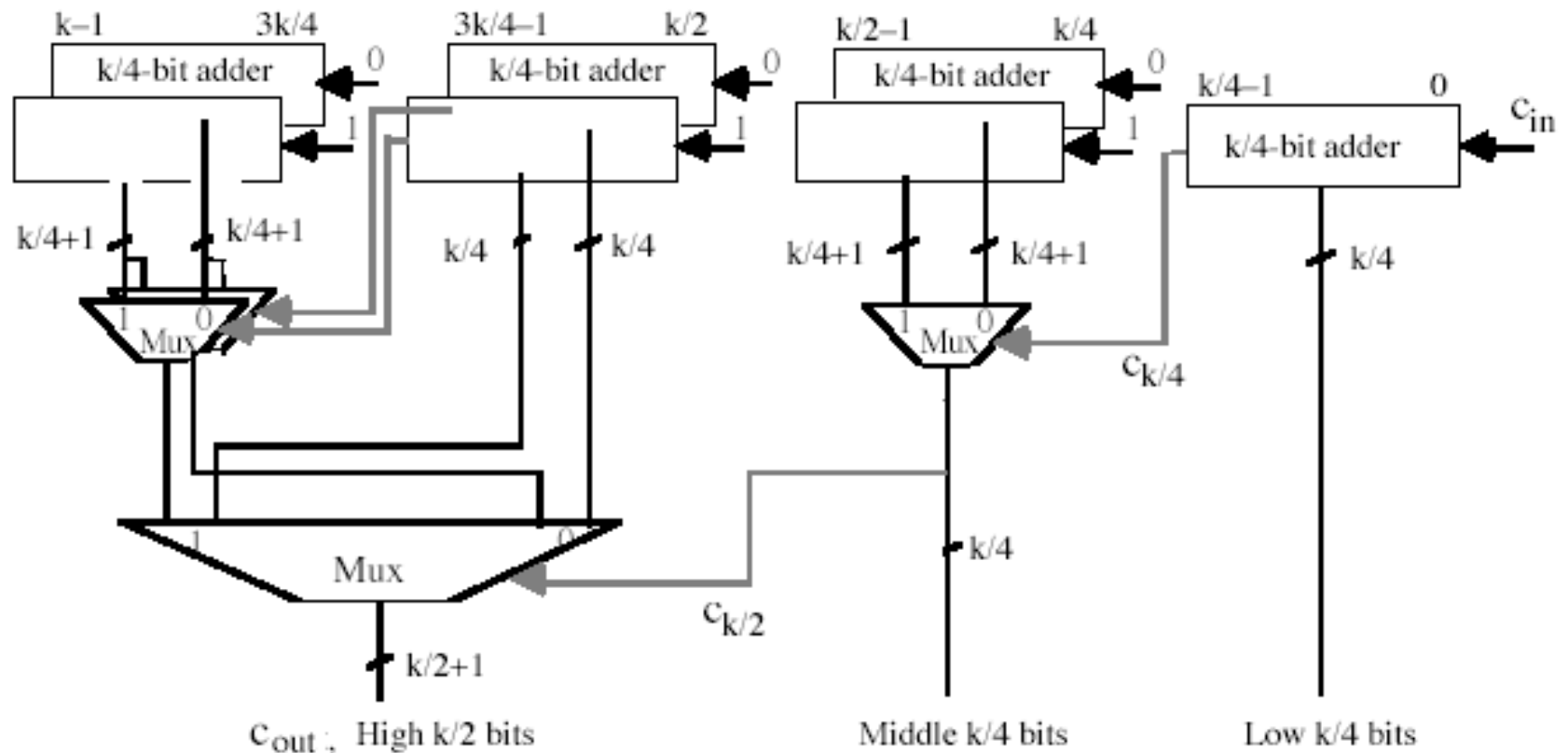


Conditional Sum Adder

- Extension of carry-select adder
- Carry select adder
 - One-level using $k/2$ -bit adders
 - Two-level using $k/4$ -bit adders
 - Three-level using $k/8$ -bit adders
 - Etc.
- Assuming k is a power of two, eventually have an extreme where there are $\log_2 k$ -levels using 1-bit adders
 - This is a **conditional sum adder**

Top-Level Block for One Bit Position

 

Three Levels of a Conditional Sum Adder

 


- branch point
- concatenation

block carry-in
determines selection

Full Adder - Revisited

Reformulate basic adder stage:

 

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Cout} = A.B + (A \oplus B).\text{Cin}$$

$$\begin{aligned} c_{i+1} &= g_i + p_i c_i \\ s_i &= p_i \oplus c_i \end{aligned}$$

$a_i \ b_i$	c_i	S_i	c_{i+1}	Carry Status
0 0	0	0	0	Delete (Carry)
	1	1	0	
0 1	0	1	0	Propagate (Carry-in)
	1	0	1	
	0	1	0	
	1	0	1	
1 1	0	0	1	Generate (Carry-out)
	1	1	1	

carry “propagate”

$$p_i = a_i \oplus b_i$$

carry “generate”


$$g_i = a_i b_i$$

Carry Look Ahead Adder

- Calculates the carry signals in advance, based on the input signals
- Define two additional signals g_i and p_i
- g_i is the *generate* bit, which is 1 only if the carry out is to be generated irrespective of the input carry. This is the case, when both inputs are high
- p_i is the *propagate* bit, which is 1 only if the output carry is to be same as input carry, i.e. $c_i = c_{i+1}$. This is the case, when only one of the two inputs is high.
- Thus the carry out of i th stage can be expressed as $c_{i+1} = g_i + p_i c_i$

Carry Look-ahead Adders

- Ripple adder using p and g signals:

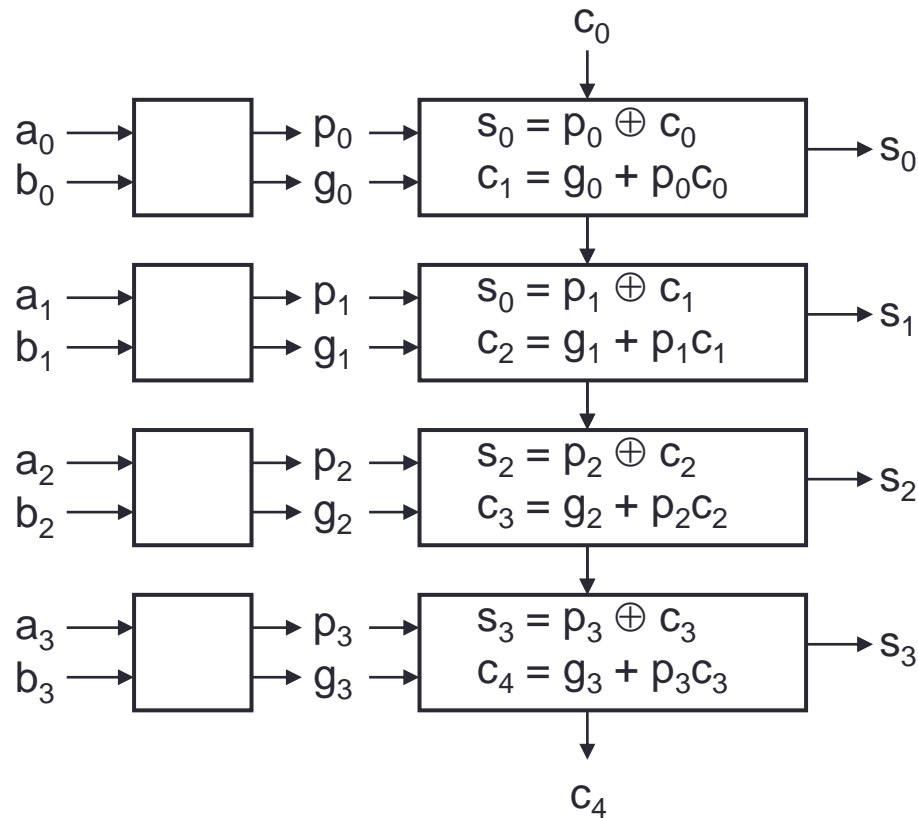

- So far, no advantage over ripple adder: $T \propto N$

Carry Look-ahead Adders

- If $C_4=1$, then either:

- g_3 generated at bit pos 3
- $g_2 \cdot p_3$ generated at bit pos 2, propagated 3
- $g_1 \cdot p_2 \cdot p_3$ generated at bit pos 1, propagated 2,3
- $g_0 \cdot p_1 \cdot p_2 \cdot p_3$ generated at bit pos 0, propagated 1,2,3
- $C_{in} \cdot p_0 \cdot p_1 \cdot p_2 \cdot p_3$ input carry, propagated 0,1,2,3

- $C_4 = g_3 + g_2 \cdot p_3 + g_1 \cdot p_2 \cdot p_3 + g_0 \cdot p_1 \cdot p_2 \cdot p_3 + C_{in} \cdot p_0 \cdot p_1 \cdot p_2 \cdot p_3$

- Expand carries:


$$C_0$$

$$C_1 = g_0 + p_0 C_0$$

$$C_2 = g_1 + p_1 C_1 = g_1 + p_1 g_0 + p_1 p_0 C_0$$

$$C_3 = g_2 + p_2 C_2 = g_2 + p_2 g_1 + p_1 p_2 g_0 + p_2 p_1 p_0 C_0$$

 
$$C_4 = g_3 + p_3 C_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$$



Four-Bit Carry Look-ahead Adder

Complexity
reduced by
deriving the
carry-out
indirectly

 Full carry look-ahead is quite practical
for a 4-bit adder



Carry Look-ahead Beyond 4 Bits

Consider a 32-bit adder

$$c_1 = g_0 \mid c_0 p_0$$

$$c_2 = g_1 \mid g_0 p_1 \mid c_0 p_0 p_1$$

$$c_3 = g_2 \mid g_1 p_2 \mid g_0 p_1 p_2 \mid c_0 p_0 p_1 p_2$$

⋮
⋮
⋮

$$c_{31} = g_{30} \mid g_{29} p_{30} \mid g_{28} p_{29} p_{30} \mid g_{27} p_{28} p_{29} p_{30} \mid \dots \mid c_0 p_0 p_1 p_2 p_3 \dots p_{29} p_{30}$$

32-input AND

32-input OR

High fan-ins necessitate
tree-structured circuits


Two Solutions to the Fan-in Problem

- High-radix addition (i.e., radix 2^h)
Increases the latency for generating g and p signals and sum digits, but simplifies the carry network
- Multilevel look-ahead
- Example: 16-bit addition
Radix-16 (four digits)
Two-level carry look-ahead (four 4-bit blocks)
- Either way, the carries c_4 , c_8 , and c_{12} are determined first

c_{16}	c_{15}	c_{14}	c_{13}	c_{12}	c_{11}	c_{10}	c_9	c_8	c_7	c_6	c_5	c_4	c_3	c_2	c_1	c_0
c_{out}				?				?				?				c_{in}

Multilevel CLA

 - “Group” propagate and generate signals:
- P true if the group as a whole propagates a carry to c_{out}
- G true if the group as a whole generates a carry
- Group P and G can be generated hierarchically.



$$P = p_i p_{i+1} \dots p_{i+k}$$

$$G = g_{i+k} + p_{i+k}g_{i+k-1} + \dots + (p_{i+1}p_{i+2} \dots p_{i+k})g_i$$

$$C_{out} = G + PC_{in}$$


C_{in}

↓



↓

C_{out}

CLA: N-Bit Architecture

 

A Building Block for Multilevel CLA

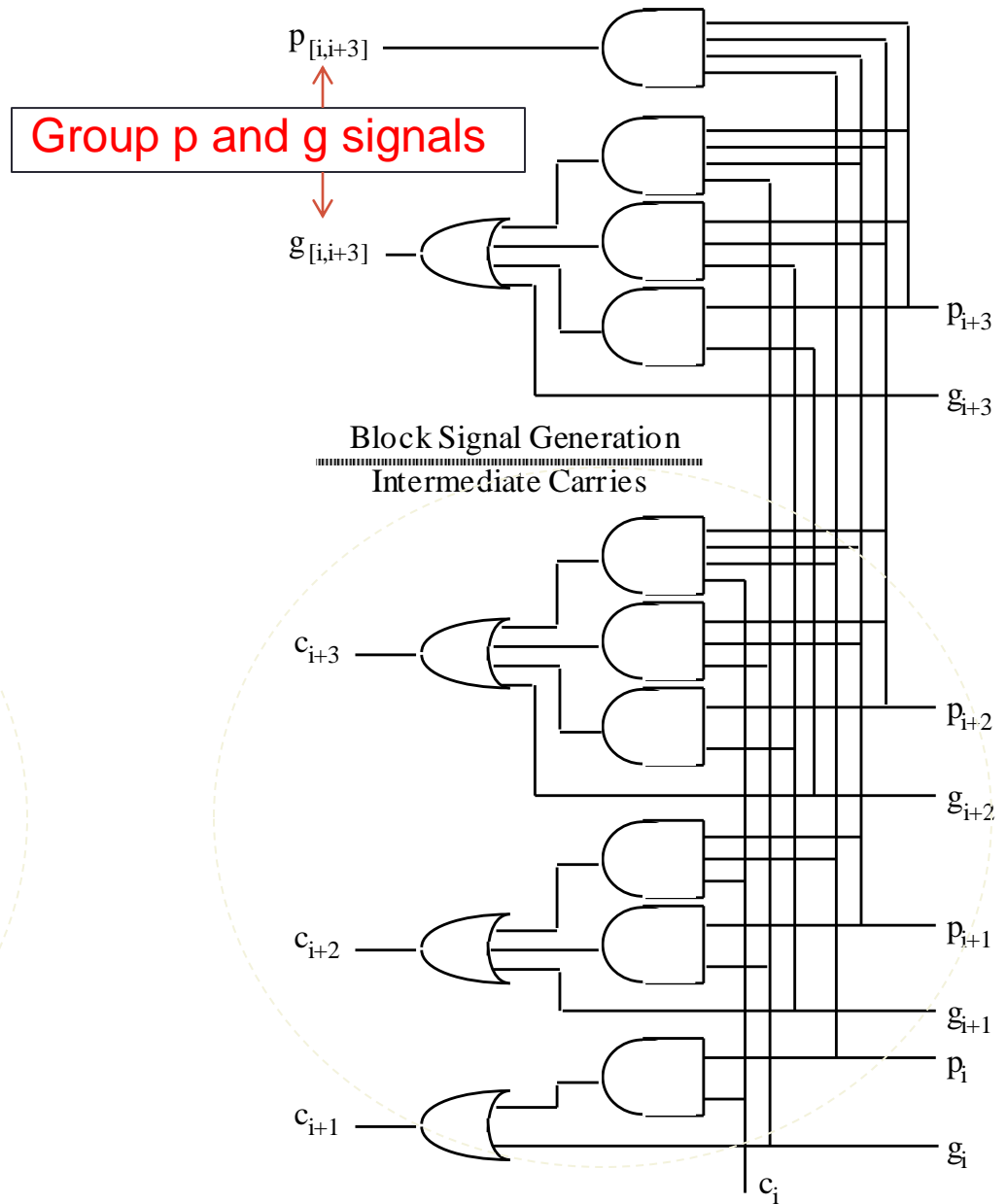 

A 4-bit CLA group network

12-Bit CLA

A= 1101


B= 0111

1001

0110

1010


1101

 

T=0	0	0000	0	0000	0	0000
T=2	1	0100	0	1111	1	0111
T=3	1	0100	1	0000	1	0111
T=4	1	0101	1	0000	1	0111

Summary: Carry Look-ahead Adder

 - CLA compared to ripple-carry adder:
 - Faster
but delay still linear (w.r.t. # of bits)
 - Larger area
 - P, G signal generation
 - Carry generation circuits
 - Carry generation circuit for each bit position (no re-use)
- Limitation: cannot go beyond 4 bits of look-ahead
 - Large p,g fan-out slows down carry generation
- Non-Uniform Lay-out



References

- The contents of this lecture are courtesy of
 - Kia Bazargan
 - Behrooz Parhami
 - Kris Gaj
 - Sukumar Ghosh
 - Narjis Fatima



Write down Verilog Code to swap three numbers on falling clock edge, (none of them retains its previous value). The circuit should have a synchronous reset.

Give most optimum level implementation of a 25-bit Non-uniform Carry Select Adder. Compare the results with uniform Carry Select Adder.

Point out the errors in the following Verilog code

```
always @ (*) begin
if (sel == 2'b00) begin
out_a = 2'b01;
out_b = 2'b10; end
else out_a = 2'b01; end
```

Code the logic of following equations in Verilog. All variables are two bit wide

```
acc0 = acc1 + in1;
acc1 = acc0 + in2;
out = acc0 + acc1;
```

Write down Verilog Code of a circuit that produces a series of Fibonacci numbers (0,1,2,3,5,8....). The only inputs to the circuit are clock and reset. The output is 5-bits. Assume the reset is asserted at start.

Give most optimum level implementation of an 18-bit Non-uniform Carry Select Adder. Compare the results with uniform Carry Select Adder.

Point out the mistake in the following Verilog code

```
always@(a or b or c)
case(a)
  2'b11 : e = b;
  2'b10 : e = ~c;
end case
```

Write a Verilog description for a circuit that accepts a 4-bit input and outputs true if the input is a Fibonacci number